

## T3-9.11 Short Circuit Admittance Parameter

VISVESVARAYA TECHNOLOGICAL UNIVERSITY, BELAGAVI  
 B.E: Electronics & Communication Engineering / B.E: Electronics & Telecommunication Engineering  
 NEP, Outcome Based Education (OBE) and Choice Based Credit System (CBCS)  
 (Effective from the academic year 2021 – 22)

### IV Semester

Circuits & Controls			
Course Code	21EC43	CIE Marks	50
Teaching Hours/Week (L: T: P: S)	(3:0:2:0)	SEE Marks	50
Total Hours of Pedagogy	40 hours Theory + 13 Lab slots	Total Marks	100
Credits	04	Exam Hours	03

Module-1	
<b>Basic concepts and network theorems</b> Types of Sources, Loop analysis, Nodal analysis with independent DC and AC Excitations. (Textbook 1: 2.3, 4.1, 4.2, 4.3, 4.4, 10.6) Super position theorem, Thevenin's theorem, Norton's Theorem, Maximum Power transfer Theorem. (Textbook 2: 9.2, 9.4, 9.5, 9.7)	
<b>Teaching-Learning Process</b>	Chalk and Talk, YouTube videos, Demonstrate the concepts using circuits <b>RBT Level: L1, L2, L3</b>

Module-2	
<b>Two port networks:</b> Short- circuit Admittance parameters, Open- circuit Impedance parameters, Transmission parameters, Hybrid parameters (Textbook 3: 11.1, 11.2, 11.3, 11.4, 11.5) <b>Laplace transform and its Applications:</b> Step Ramp, Impulse, Solution of networks using Laplace transform, Initial value and final value theorem (Textbook 3: 7.1, 7.2, 7.4, 7.7, 8.4)	
<b>Teaching-Learning Process</b>	Chalk and Talk <b>RBT Level: L1, L2, L3</b>

Module-3	
<b>Basic Concepts and representation:</b> Types of control systems, effect of feedback systems, differential equation of physical systems (only electrical systems), Introduction to block diagrams, transfer functions, Signal Flow Graphs (Textbook 4: Chapter 1.1, 2.2, 2.4, 2.5, 2.6)	
<b>Teaching-Learning Process</b>	Chalk and Talk, YouTube videos <b>RBT Level: L1, L2, L3</b>


Module-4	
<b>Time Response analysis:</b> Time response of first order systems. Time response of second order systems, time response specifications of second order systems (Textbook 4: Chapter 5.3, 5.4) <b>Stability Analysis:</b> Concepts of stability necessary condition for stability, Routh stability criterion, relative stability Analysis (Textbook 4: Chapter 5.3, 5.4, 6.1, 6.2, 6.4, 6.5)	
<b>Teaching-Learning Process</b>	Chalk and Talk, Any software tool to show time response <b>RBT Level: L1, L2, L3</b>

Module-5	
<b>Root locus:</b> Introduction the root locus concepts, construction of root loci (Textbook 4: 7.1, 7.2, 7.3)	
<b>Frequency Domain analysis and stability:</b> Correlation between time and frequency response and Bode plots (Textbook 4: 8.1, 8.2, 8.4)	
<b>State Variable Analysis:</b> Introduction to state variable analysis: Concepts of state, state variable and state models. State model for Linear continuous -Time systems, solution of state equations. (Textbook 4: 12.2, 12.3, 12.6)	
<b>Teaching-Learning Process</b>	Chalk and Talk, Any software tool to plot Root locus, Bode plot <b>RBT Level:</b> L1, L2, L3

**Suggested Learning Resources:****Text Books**

1. Engineering circuit analysis, William H Hayt, Jr, Jack E Kemmerly, Steven M Durbin, Mc Graw Hill Education, Indian Edition 8e.
2. Networks and Systems, D Roy Choudhury, New age international Publishers, second edition.
3. Network Analysis, M E Van Valkenburg, Pearson, 3e.
4. Control Systems Engineering, I J Nagrath, M. Gopal, New age international Publishers, Fifth edition.
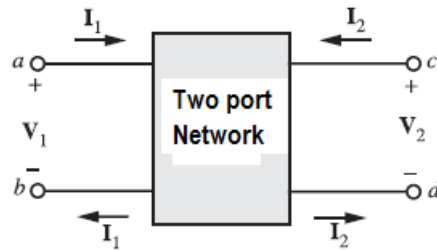
## 2) Short circuit Admittance or Y- parameters



Consider the variables  $I_1$  &  $I_2$  as dependent variable and

$V_1$  &  $V_2$  as independent variables.

The coefficients of independent variables,  $V_1$  and  $V_2$  are called as **Y parameters**.


Hence, the two equations that describe the two-port network are

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$


$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

Putting the above equations in matrix form, we get
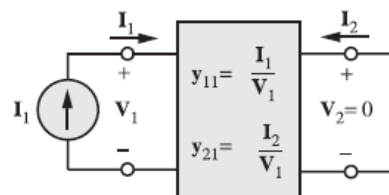
$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$


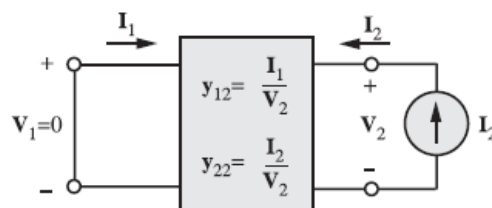
$$Y_{11} = \frac{I_1}{V_1}, \text{ when } V_2 = 0 \quad Y_{21} = \frac{I_2}{V_1}, \text{ when } V_2 = 0$$



$$Y_{12} = \frac{I_1}{V_2}, \text{ when } V_1 = 0 \quad Y_{22} = \frac{I_2}{V_2}, \text{ when } V_1 = 0$$

$$\underbrace{Y_{11} \ Y_{12} \ Y_{21} \ Y_{22}}_{\text{Y parameters : unit - mho}}$$

The SI unit of admittance is the **SIEMENS (symbol S)**; the older, synonymous unit is mho, and its symbol is  $\mathcal{U}$

Y parameters are called as **admittance parameters** because these are simply, the ratios of currents and voltages. Units of Y parameters are mho.

We can calculate two Y parameters,  $Y_{11}$  and  $Y_{21}$  by doing short circuit of port2.


Similarly, we can calculate the other two Y parameters,  $Y_{12}$  and  $Y_{22}$  by doing short circuit of port1.

Hence, the Y parameters are also called as **short-circuit admittance parameters**.

### Relationship of parameter



- 1) Open-circuit impedance (Z parameters)  $\rightarrow$  Express  $V_1, V_2 \rightarrow$  In terms of  $I_1, I_2 \rightarrow \begin{cases} V_1 = z_{11}I_1 + z_{12}I_2 \\ V_2 = z_{21}I_1 + z_{22}I_2 \end{cases}$
- 2) Short-circuit admittance (Y parameters)  $\rightarrow$  Express  $I_1, I_2 \rightarrow$  In terms of  $V_1, V_2 \rightarrow \begin{cases} I_1 = y_{11}V_1 + y_{12}V_2 \\ I_2 = y_{21}V_1 + y_{22}V_2 \end{cases}$
- 3) Transmission (T parameters)  $\rightarrow$  Express  $V_1, I_1 \rightarrow$  In terms of  $V_2, I_2 \rightarrow \begin{cases} V_1 = AV_2 - BI_2 \\ I_1 = CV_2 - DI_2 \end{cases}$
- 4) Inverse transmission (T' parameters)  $\rightarrow$  Express  $V_2, I_2 \rightarrow$  In terms of  $V_1, I_1 \rightarrow \begin{cases} V_2 = A'V_1 - B'I_1 \\ I_2 = C'V_1 - D'I_1 \end{cases}$
- 5) Hybrid (h-parameters)  $\rightarrow$  Express  $V_1, I_2 \rightarrow$  In terms of  $I_1, V_2 \rightarrow \begin{cases} V_1 = h_{11}I_1 + h_{12}V_2 \\ I_2 = h_{21}I_1 + h_{22}V_2 \end{cases}$
- 6) Inverse hybrid (g-parameters)  $\rightarrow$  Express  $I_1, V_2 \rightarrow$  In terms of  $V_1, I_2 \rightarrow \begin{cases} I_1 = g_{11}V_1 + g_{12}I_2 \\ V_2 = g_{21}V_1 + g_{22}I_2 \end{cases}$

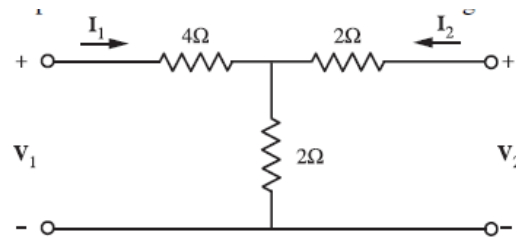**1) Determine the admittance parameters of the T network shown in Fig**



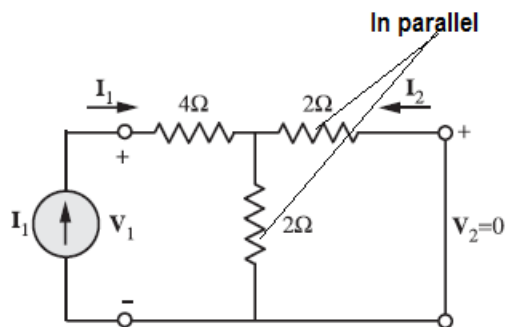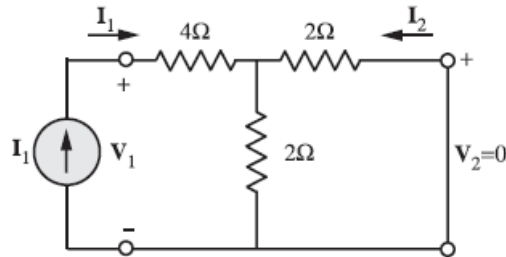
**To find  $y_{11}$  and  $y_{21}$ .**

Short the output terminals and connect a current source  $I_1$  to the input terminals.



$$I_1 = \frac{V_1}{4 + \frac{2 \times 2}{2 + 2}} = \frac{V_1}{5}$$

$$\text{Hence, } y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = \frac{1}{5} \text{ S}$$

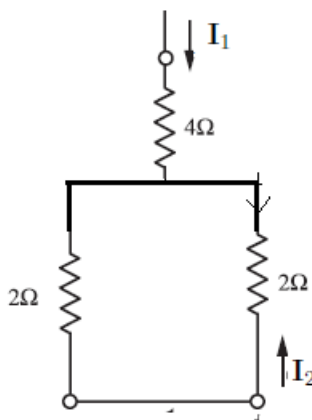

Using the principle of current division,

$$-I_2 = \frac{I_1 \times 2}{2 + 2} = \frac{I_1}{2}$$



- Negative sign flowing against actual direction

$$-I_2 = \frac{1}{2} \left[ \frac{V_1}{5} \right]$$

$$\text{Hence, } y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} = \frac{-1}{10} \text{ S}$$

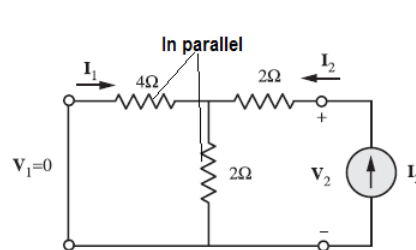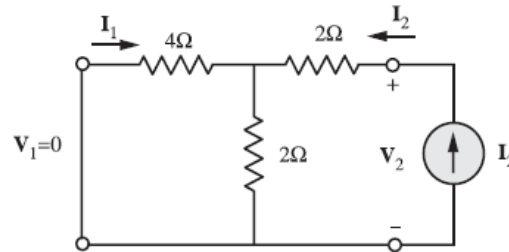**To find  $y_{12}$  and  $y_{22}$ .**


Short-circuit the input terminals and connect a current source  $I_2$  to the output terminals. The circuit so obtained is shown in Fig.



$$\begin{aligned} I_2 &= \frac{V_2}{2 + \frac{4 \times 2}{4 + 2}} \\ &= \frac{V_2}{2 + \frac{4}{3}} \\ &= \frac{3V_2}{10} \end{aligned}$$

$$\text{Hence, } y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} = \frac{3}{10} \text{ S}$$

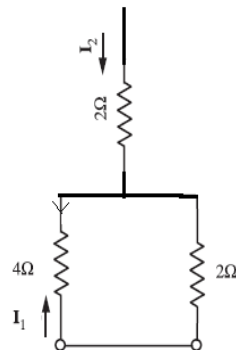Employing the principle of current division, we have



$$-I_1 = \frac{I_2 \times 2}{2 + 4}$$

$$-I_1 = \frac{2I_2}{6}$$

$$-I_1 = \frac{1}{3} \left[ \frac{3V_2}{10} \right]$$


$$\text{Hence, } y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} = \frac{-1}{10} \text{ S}$$

It may be noted that,  $y_{12} = y_{21}$ . Thus, in matrix form we have

$$\mathbf{I} = \mathbf{YV}$$

$$\Rightarrow \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \frac{1}{5} & \frac{-1}{10} \\ \frac{-1}{10} & \frac{3}{10} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

## 2)Y- Parameter shortcut

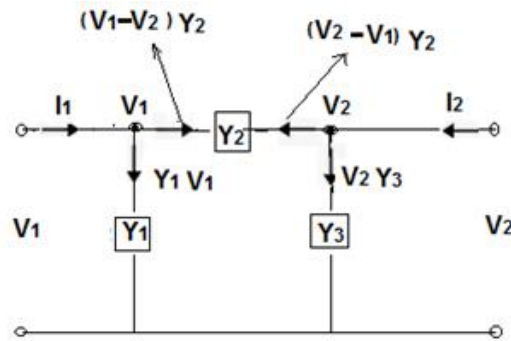

Apply KCL at the node ①

$$I_1 = Y_1 V_1 + (V_1 - V_2) Y_2$$

$$I_1 = (Y_1 + Y_2) V_1 - Y_2 V_2 \dots\dots\dots(1)$$

Apply KCL at the node ②

$$I_2 = (V_2 - V_1) Y_2 + Y_3 V_2$$

$$I_2 = -Y_2 V_1 + (Y_2 + Y_3) V_2 \dots\dots\dots(2)$$

$$I_1 = (Y_1 + Y_2) V_1 - Y_2 V_2 \dots\dots\dots(1)$$

Compare the co efficients of  $V_1$  &  $V_2$ 

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$Y_{11} = (Y_1 + Y_2)$$

$$Y_{12} = Y_{21} = -Y_2$$

$$I_2 = -Y_2 V_1 + (Y_2 + Y_3) V_2 \dots\dots\dots(2)$$


Compare the co efficients of  $V_1$  &  $V_2$ 

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

$$Y_{22} = (Y_2 + Y_3)$$

$$Y_{12} = Y_{21} = -Y_2$$
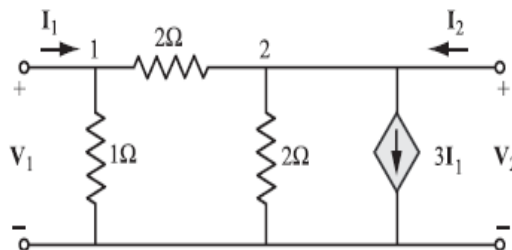
## 3) Find y and z parameters for the network shown in Fig. which contains a current controlled source.



Apply KCL at node 1 and 2

$$\text{At node 1,} \quad 1.5V_1 - 0.5V_2 = I_1$$

$$\text{At node 2,} \quad -0.5V_1 + V_2 = I_2 - 3I_1$$

In matrix form,

$$\begin{bmatrix} 1.5 & -0.5 \\ -0.5 & 1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ -3 & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 1.5 & -0.5 \\ -0.5 & 1 \end{bmatrix}^{-1} \begin{bmatrix} 1 & 0 \\ -3 & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Therefore,


$$= \begin{bmatrix} -0.4 & 0.4 \\ -3.2 & 1.2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$[z] = \begin{bmatrix} -0.4 & 0.4 \\ -3.2 & 1.2 \end{bmatrix}$$

$$[y] = [z]^{-1} = \begin{bmatrix} 1.5 & -0.5 \\ 4 & -0.5 \end{bmatrix}$$


$$[y] = \frac{1}{[z]}$$

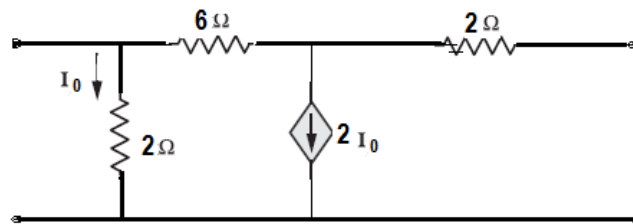3) Obtain the Y- parameter of the circuit shown



Case –(1) to find  $Y_{11}$  and  $Y_{21}$

$$y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} \quad y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

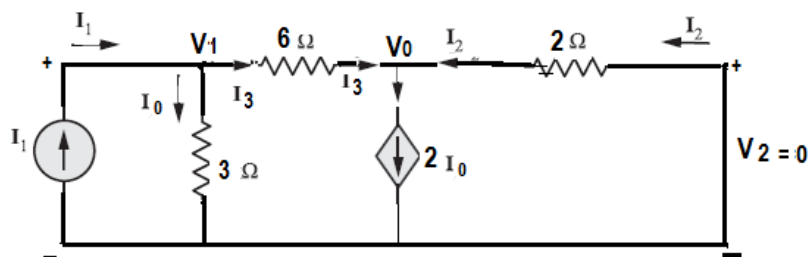



At node-1 Apply KCL

$$I_1 = I_0 + I_3$$

$$I_1 = \frac{V_1}{3} + \frac{V_1 - V_0}{6} \quad \dots\dots\dots(1)$$

At Node 2 Apply KCL

$$I_3 + I_2 = 2 I_0$$

$$\begin{aligned} \frac{V_1 - V_0}{6} + \frac{0 - V_0}{2} &= 2 \times \frac{V_1}{3} \quad \left| \quad I_0 = \frac{V_1}{3} \right. \\ V_1 - V_0 - 3V_0 &= 4V_1 \\ -4V_0 &= 3V_1 \\ V_0 &= -\frac{3}{4} V_1 \quad \dots\dots\dots(2) \end{aligned}$$

Putting the value of  $V_0$  in eq (1)

$$\begin{aligned} I_1 &= \frac{V_1}{3} + \frac{V_1 - (-\frac{3}{4} V_1)}{6} \\ &= \frac{V_1}{3} + \frac{7V_1}{24} \\ I_1 &= \frac{16}{24} V_1 \quad \dots\dots\dots(3) \\ Y_{11} &= \frac{I_1}{V_1} = \frac{16}{24} \end{aligned}$$


$$\begin{aligned} Y_{21} &= \frac{I_2}{V_1} \\ &= \frac{-V_0}{2 V_1} \\ &= \frac{-(-\frac{3}{4} V_1)}{2} \\ Y_{21} &= \frac{3}{8} \end{aligned}$$

REFERENCE

$$\begin{aligned} I_2 &= \frac{0 - V_0}{2} = \frac{-V_0}{2} \\ V_0 &= -\frac{3}{4} V_1 \quad \dots\dots\dots(2) \end{aligned}$$

Case -(2) to find  $Y_{22}$  and  $Y_{12}$

$$y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} \quad y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$

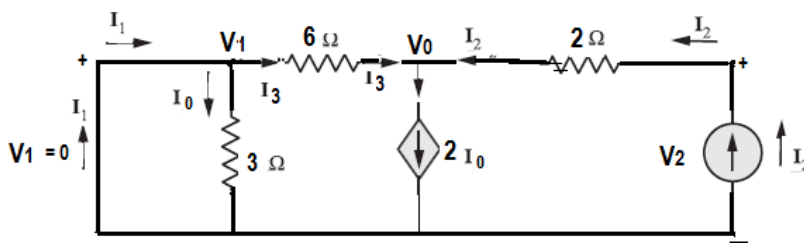

At node-1 Apply KCL

$$\begin{aligned}
 I_1 &= i0 + i3 \\
 &= 0 + \frac{V1 - V_o}{6} \\
 &= 0 + \frac{-V_o}{6} \\
 I_1 &= \frac{-V_o}{6} \dots (1)
 \end{aligned}$$

At node-2 Apply KCL

$$\begin{aligned}
 I_3 + I_2 &= 2 I_o \\
 \frac{V1 - V_o}{6} + I_2 &= 0 \\
 \frac{0 - V_o}{6} + I_2 &= 0 \\
 I_2 &= \frac{V_o}{6} \dots (2)
 \end{aligned}$$

From the diagram

$$I_2 = \frac{V2 - V_o}{2} \dots (3)$$

Comparing Eq.2 and 3

$$\frac{V_o}{6} = \frac{V2 - V_o}{2}$$

$$V_o = 3V2 - 3V_o$$

$$3V2 = 4V_o$$

$$V2 = \frac{4}{3} V_o \dots (4)$$

From the diagram

$$I_2 = \frac{V2 - V_o}{2} \dots (3)$$

$$y_{12} = \frac{I_1}{V_2} = \frac{\frac{-V_o}{6}}{\frac{4}{3} V_o} = -\frac{1}{8} = -0.1258$$

Comparing Eq.2 and 3

$$\frac{V_o}{6} = \frac{V2 - V_o}{2}$$

$$V_o = 3V2 - 3V_o$$

$$3V2 = 4V_o$$

$$V2 = \frac{4}{3} V_o \dots (4)$$

$$y_{22} = \frac{I_2}{V_2} = \frac{\frac{V_o}{6}}{\frac{4}{3} V_o} = \frac{1}{8} = 0.125$$

Reference

$$V2 = \frac{4}{3} V_o \dots (4)$$

$$I_2 = \frac{V_o}{6} \dots (2)$$

.....

**RELATION BETWEEN PARAMETERS**

Table - Parameter relationships				
	z	y	T	h
z	$\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix}$	$\begin{bmatrix} \frac{y_{22}}{\Delta y} & \frac{-y_{12}}{\Delta y} \\ \frac{-y_{21}}{\Delta y} & \frac{y_{11}}{\Delta y} \end{bmatrix}$	$\begin{bmatrix} \frac{A}{C} & \frac{\Delta T}{C} \\ \frac{1}{C} & \frac{D}{C} \end{bmatrix}$	$\begin{bmatrix} \frac{\Delta h}{h_{22}} & \frac{h_{12}}{h_{22}} \\ \frac{-h_{21}}{h_{22}} & \frac{1}{h_{22}} \end{bmatrix}$
y	$\begin{bmatrix} \frac{z_{22}}{\Delta z} & \frac{-z_{12}}{\Delta z} \\ \frac{-z_{21}}{\Delta z} & \frac{z_{11}}{\Delta z} \end{bmatrix}$	$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$	$\begin{bmatrix} \frac{D}{B} & \frac{-\Delta T}{B} \\ \frac{-1}{B} & \frac{A}{B} \end{bmatrix}$	$\begin{bmatrix} \frac{1}{h_{11}} & \frac{-h_{22}}{h_{11}} \\ \frac{h_{21}}{h_{11}} & \frac{\Delta h}{h_{11}} \end{bmatrix}$
T	$\begin{bmatrix} \frac{z_{11}}{z_{21}} & \frac{\Delta z}{z_{21}} \\ \frac{1}{z_{21}} & \frac{z_{22}}{z_{21}} \end{bmatrix}$	$\begin{bmatrix} \frac{-y_{22}}{y_{21}} & \frac{-1}{y_{21}} \\ \frac{-\Delta y}{y_{21}} & \frac{-y_{11}}{y_{21}} \end{bmatrix}$	$\begin{bmatrix} A & B \\ C & D \end{bmatrix}$	$\begin{bmatrix} \frac{-\Delta h}{h_{21}} & \frac{-h_{11}}{h_{21}} \\ \frac{-h_{22}}{h_{21}} & \frac{-1}{h_{21}} \end{bmatrix}$
h	$\begin{bmatrix} \frac{\Delta z}{z_{22}} & \frac{z_{12}}{z_{22}} \\ \frac{-z_{21}}{z_{22}} & \frac{1}{z_{22}} \end{bmatrix}$	$\begin{bmatrix} \frac{1}{y_{11}} & \frac{-y_{12}}{y_{11}} \\ \frac{y_{21}}{y_{11}} & \frac{\Delta y}{y_{11}} \end{bmatrix}$	$\begin{bmatrix} \frac{B}{D} & \frac{\Delta T}{D} \\ \frac{-1}{D} & \frac{C}{D} \end{bmatrix}$	$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix}$
$\Delta z = z_{11}z_{22} - z_{12}z_{21}, \Delta y = y_{11}y_{22} - y_{12}y_{21}, \Delta h = h_{11}h_{22} - h_{12}h_{21}, \Delta T = AD - BC$				

4) Determine the y parameters for a two-port network if the z parameters are

$$z = \begin{bmatrix} 10 & 5 \\ 5 & 9 \end{bmatrix}$$

$$\Delta z = \begin{vmatrix} 10 & 5 \\ 5 & 9 \end{vmatrix}$$

$$\Delta z = 10 \times 9 - 5 \times 5 = 65$$

$$y_{11} = \frac{z_{22}}{\Delta z} = \frac{9}{65} \text{S}$$

$$y_{12} = \frac{-z_{12}}{\Delta z} = \frac{-5}{65} \text{S}$$

$$y_{21} = \frac{-z_{21}}{\Delta z} = \frac{-5}{65} \text{S}$$

$$y_{22} = \frac{z_{11}}{\Delta z} = \frac{10}{65} \text{S}$$

BY THE RELATION

$$\begin{bmatrix} \frac{z_{22}}{\Delta z} & \frac{-z_{12}}{\Delta z} \\ \frac{-z_{21}}{\Delta z} & \frac{z_{11}}{\Delta z} \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$$