

T-2 9.4 THEVENIN'S THEOREM

VISVESVARAYA TECHNOLOGICAL UNIVERSITY, BELAGAVI
 B.E: Electronics & Communication Engineering / B.E: Electronics & Telecommunication Engineering
 NEP, Outcome Based Education (OBE) and Choice Based Credit System (CBCS)
 (Effective from the academic year 2021 – 22)

IV Semester

Circuits & Controls			
Course Code	21EC43	CIE Marks	50
Teaching Hours/Week (L: T: P: S)	(3:0:2:0)	SEE Marks	50
Total Hours of Pedagogy	40 hours Theory + 13 Lab slots	Total Marks	100
Credits	04	Exam Hours	03

Module-1	
Basic concepts and network theorems Types of Sources, Loop analysis, Nodal analysis with independent DC and AC Excitations. (Textbook 1: 2.3, 4.1, 4.2, 4.3, 4.4, 10.6) Super position theorem, Thevenin's theorem, Norton's Theorem, Maximum Power transfer Theorem. (Textbook 2: 9.2, 9.4, 9.5, 9.7)	
Teaching-Learning Process	Chalk and Talk, YouTube videos, Demonstrate the concepts using circuits RBT Level: L1, L2, L3

Module-2	
Two port networks: Short- circuit Admittance parameters, Open- circuit Impedance parameters, Transmission parameters, Hybrid parameters (Textbook 3: 11.1, 11.2, 11.3, 11.4, 11.5) Laplace transform and its Applications: Step Ramp, Impulse, Solution of networks using Laplace transform, Initial value and final value theorem (Textbook 3: 7.1, 7.2, 7.4, 7.7, 8.4)	
Teaching-Learning Process	Chalk and Talk RBT Level: L1, L2, L3

Module-3	
Basic Concepts and representation: Types of control systems, effect of feedback systems, differential equation of physical systems (only electrical systems), Introduction to block diagrams, transfer functions, Signal Flow Graphs (Textbook 4: Chapter 1.1, 2.2, 2.4, 2.5, 2.6)	
Teaching-Learning Process	Chalk and Talk, YouTube videos RBT Level: L1, L2, L3

Module-4	
Time Response analysis: Time response of first order systems. Time response of second order systems, time response specifications of second order systems (Textbook 4: Chapter 5.3, 5.4) Stability Analysis: Concepts of stability necessary condition for stability, Routh stability criterion, relative stability Analysis (Textbook 4: Chapter 5.3, 5.4, 6.1, 6.2, 6.4, 6.5)	
Teaching-Learning Process	Chalk and Talk, Any software tool to show time response RBT Level: L1, L2, L3

Module-5	
Root locus: Introduction the root locus concepts, construction of root loci (Textbook 4: 7.1, 7.2, 7.3) Frequency Domain analysis and stability: Correlation between time and frequency response and Bode plots (Textbook 4: 8.1, 8.2, 8.4) State Variable Analysis: Introduction to state variable analysis: Concepts of state, state variable and state models. State model for Linear continuous –Time systems, solution of state equations. (Textbook 4: 12.2, 12.3, 12.6)	
Teaching-Learning Process	Chalk and Talk, Any software tool to plot Root locus, Bode plot RBT Level: L1, L2, L3

Suggested Learning Resources:**Text Books**

1. Engineering circuit analysis, William H Hayt, Jr, Jack E Kemmerly, Steven M Durbin, Mc Graw Hill Education, Indian Edition 8e.
2. Networks and Systems, D Roy Choudhury, New age international Publishers, second edition.
3. Network Analysis, M E Van Valkenburg, Pearson, 3e.
4. Control Systems Engineering, I J Nagrath, M. Gopal, New age international Publishers, Fifth edition.


9.4 THEVENIN'S THEOREM

“A linear and bidirectional two- terminal network can be replaced by an equivalent network consisting of voltage source V_{TH} connected in series with a resistor R_{TH} ”

V_{TH} \longrightarrow Open circuit voltage at the terminals


R_{TH} \longrightarrow Input / Equivalent resistance at the terminals

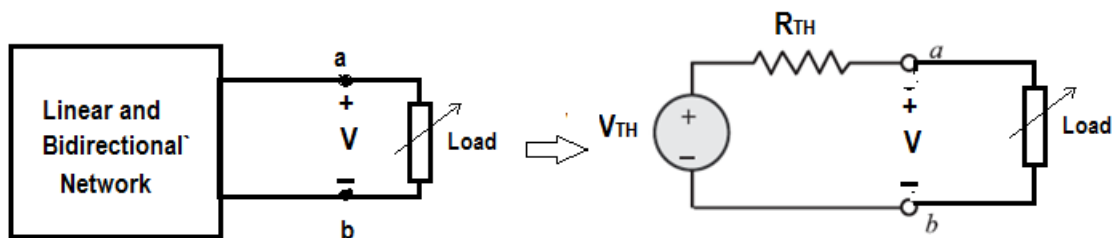
$R_{TH} \longrightarrow$ is the ratio of open-circuit voltage to the short-circuit current at the terminal pair. $R_{TH} = \frac{V_{OC}}{I_{SC}}$




STEPS TO FIND V_{TH} AND R_{TH}

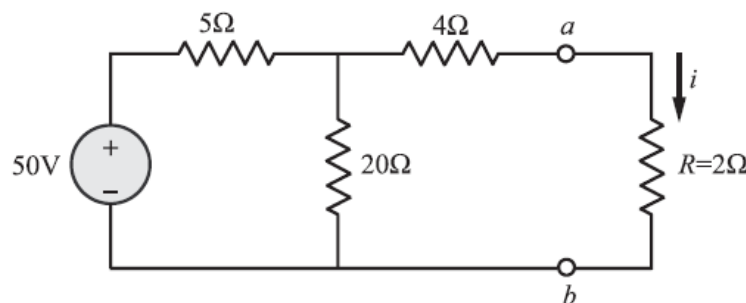- 1) Remove the load resistor and mark the terminals
 - 2) Find the open circuit voltage (V_{TH}) using KVL
 - 3) Deactivate all the independent sources and find R_{TH}
 - 4) Produce the thevenin's equivalent circuit reconnecting the load resistor.
 - 5) Find the current through the resistor.
- 1) Using the Thevenin's theorem, find the current i through $R = 2\Omega$. Refer Fig.





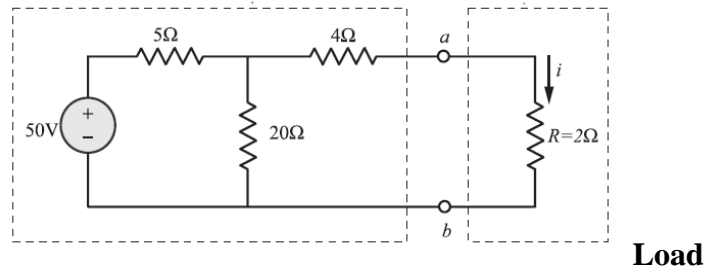

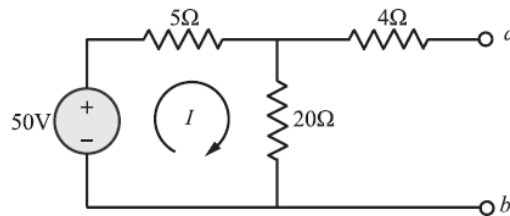After removing the load resistance the circuit is




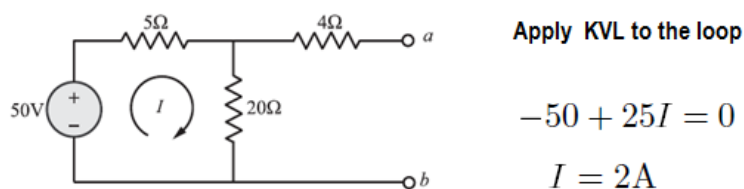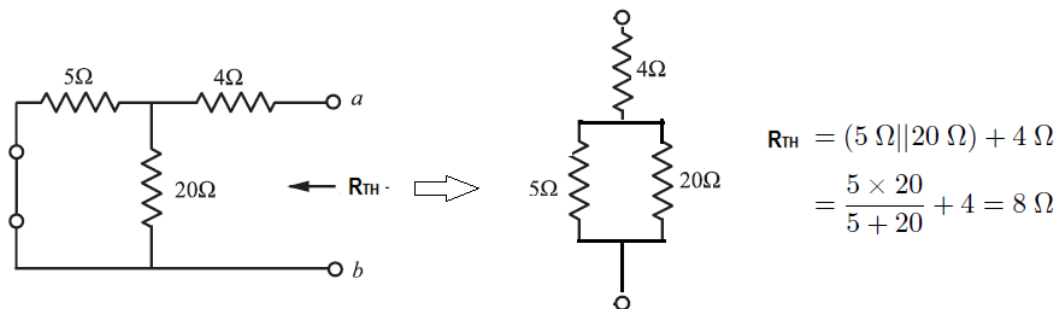
To find R_{TH} deactivate the independent voltage source.





$$V_{ab} = V_{oc} = 20(I) = 40V$$

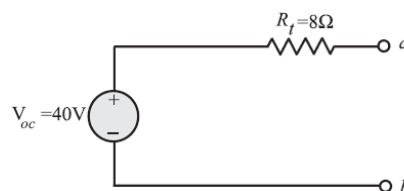Thevenin's equivalent circuit which is as shown



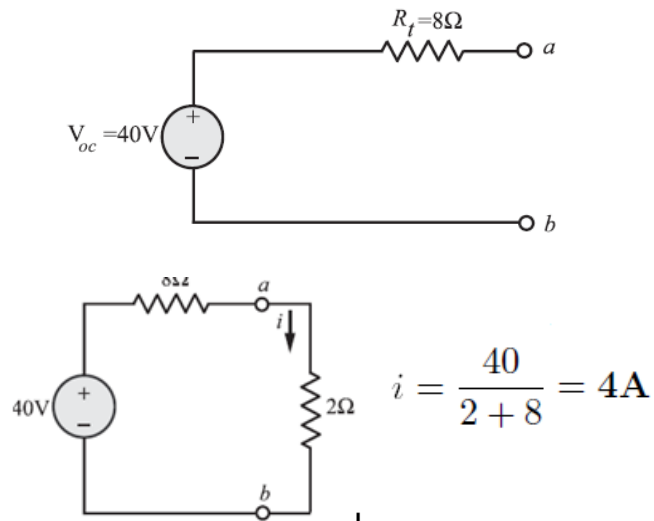

2) Find the thevenin Equivalent circuit

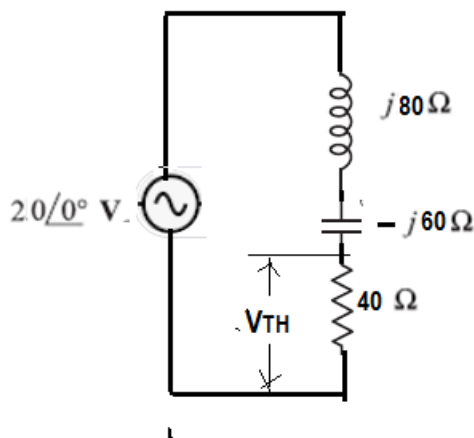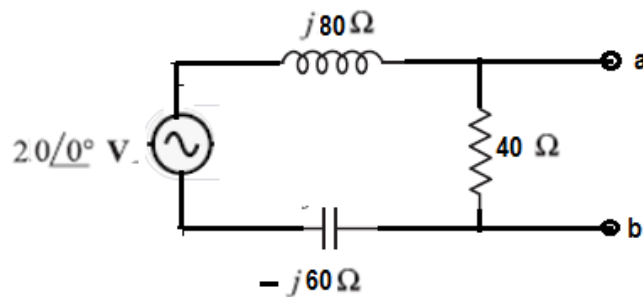



Apply voltage divider technic

$$V_{TH} = 20\angle 0^\circ \times \frac{40}{40 + j80 - j60}$$

$$= 20\angle 0^\circ \times \frac{40}{40 + j20}$$


$$= 20\angle 0^\circ \times \frac{2}{(2 + j)}$$

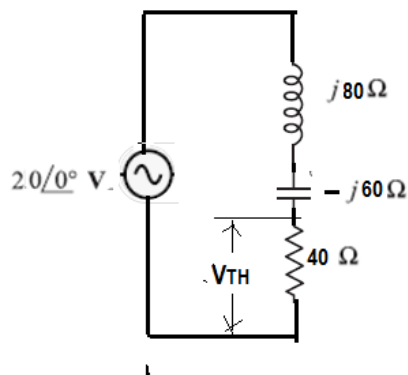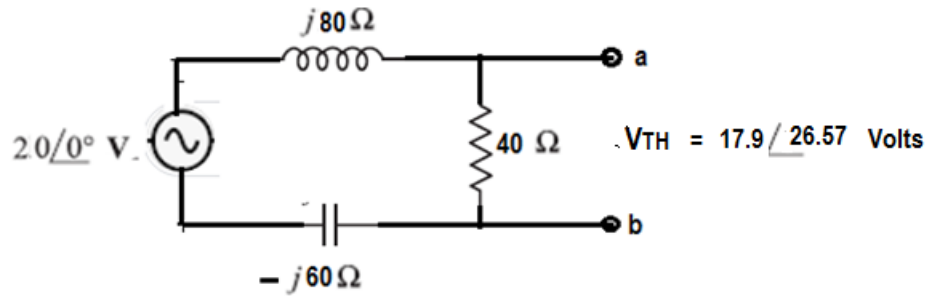
$$V_{TH} = \frac{40\angle 0^\circ}{(2 + j)} = 17.9\angle 26.57 \text{ Volts}$$



Apply voltage divider technic

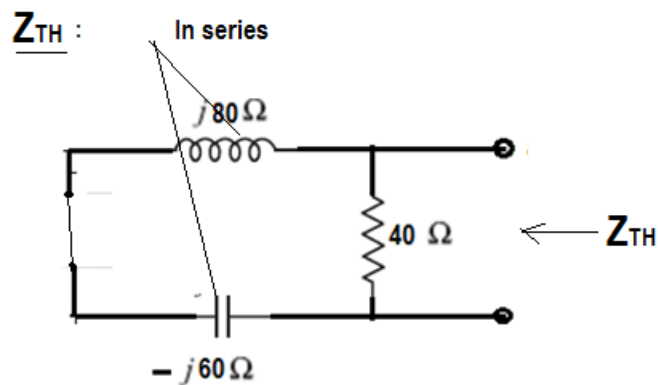
$$\begin{aligned}
 V_{TH} &= 20\angle 0^\circ \times \frac{40}{40 + j80 - j60} \\
 &= 20\angle 0^\circ \times \frac{40}{40 + j20} \\
 &= 20\angle 0^\circ \times \frac{2}{2 + j} \\
 &= \frac{40 \angle 0^\circ}{2 + j} = 17.9 \angle 26.57 \text{ Volts}
 \end{aligned}$$



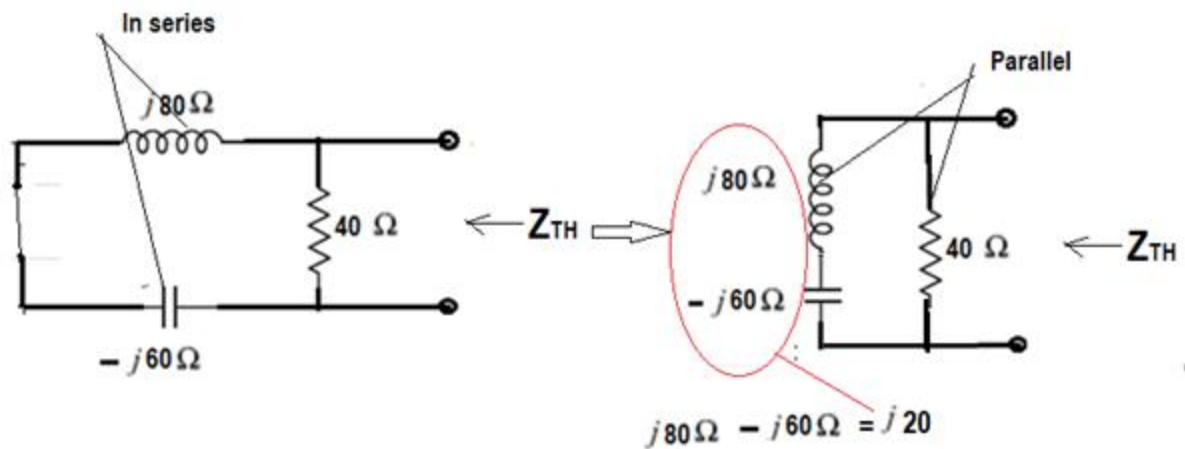


$$Z_{TH} = \frac{40 \times j20}{40 + j20} = 17.65 \angle 6.43^\circ \Omega$$

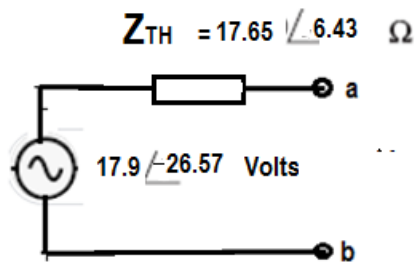Thevenin's equivalent circuit which is as shown



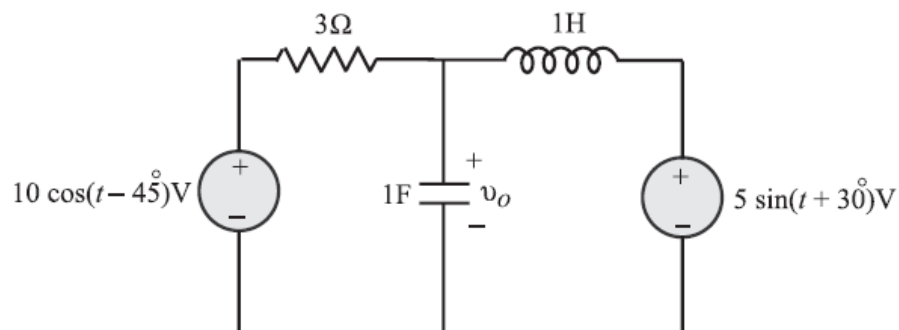3) Find V_o using Thevenin's theorem. Refer to the circuit shown in Fig



Convert the circuit given into a frequency domain equivalent or phasor circuit


$$\omega = 1$$

$$10 \cos(t - 45^\circ) \rightarrow 10 \angle -45^\circ \text{ V}$$


$$5 \sin(t + 30^\circ) = 5 \cos(t - 60^\circ) \rightarrow 5 \angle -60^\circ \text{ V}$$

$$L = 1\text{H} \rightarrow j\omega L = j \times 1 \times 1 = j1\Omega$$

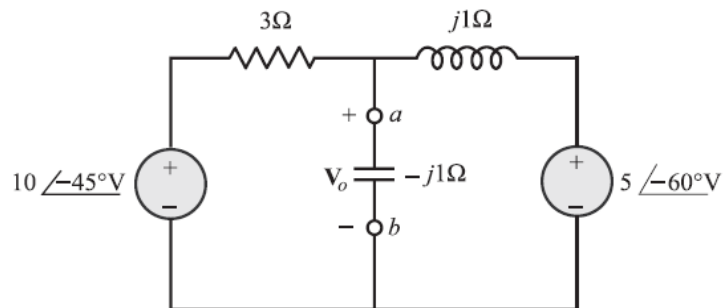
$$C = 1\text{F} \rightarrow \frac{1}{j\omega C} = \frac{1}{j \times 1 \times 1} = -j1\Omega$$




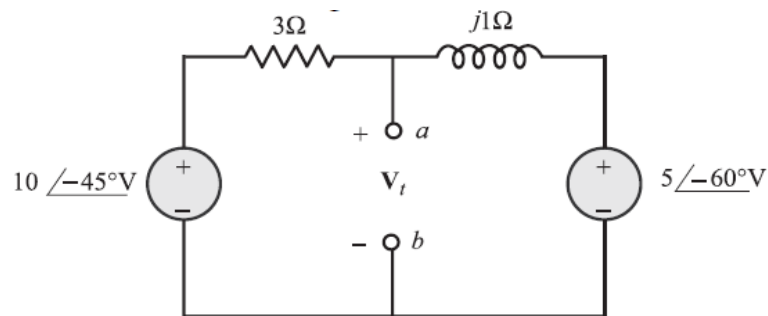
Disconnecting the capacitor from the original circuit, This circuit is used for finding V_{TH}



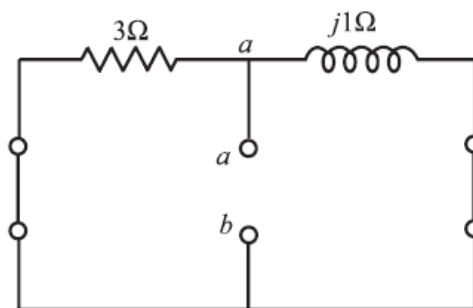
Deactivate the independent voltage sources



Apply KCL at the node a

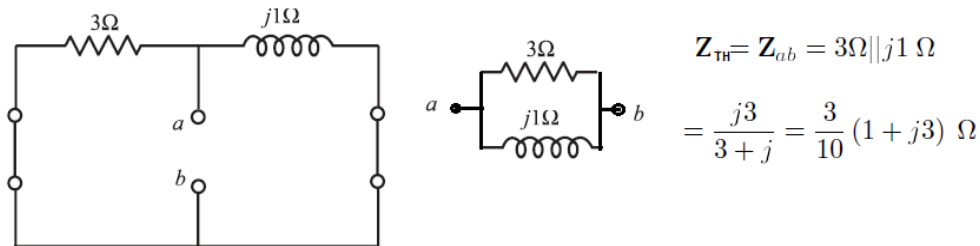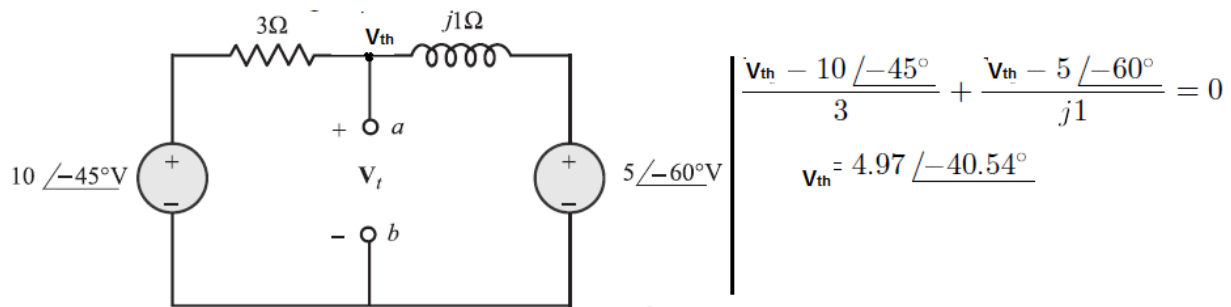

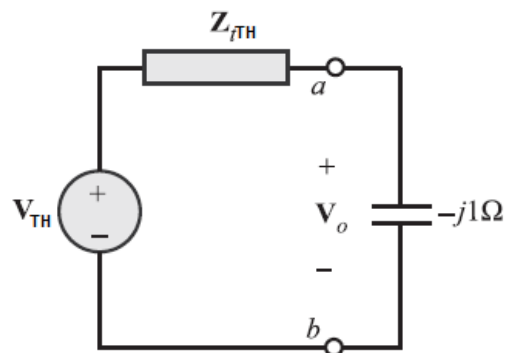Thevenin equivalent circuit along with the capacitor



Thevenin Equivalent ckt.

$$V_o = \frac{V_{TH}}{Z_t - j1}(-j1)$$

$$= \frac{4.97 \angle -40.54^\circ}{0.3(1+j3) - j1}(-j1)$$

$$= 15.73 \angle 247.9^\circ \text{ V}$$

Hence, $v_o = 15.73 \cos(t + 247.9^\circ) \text{ V}$

.....