

**T2-9.7 MAXIMUM POWER TRANSFER THEOREM****VISVESVARAYA TECHNOLOGICAL UNIVERSITY, BELAGAVI**

B.E: Electronics &amp; Communication Engineering / B.E: Electronics &amp; Telecommunication Engineering

NEP, Outcome Based Education (OBE) and Choice Based Credit System (CBCS)

(Effective from the academic year 2021 – 22)

**IV Semester**

<b>Circuits &amp; Controls</b>			
Course Code	<b>21EC43</b>	CIE Marks	50
Teaching Hours/Week (L: T: P: S)	(3:0:2:0)	SEE Marks	50
Total Hours of Pedagogy	40 hours Theory + 13 Lab slots	Total Marks	100
Credits	04	Exam Hours	03

<b>Module-1</b>	
<b>Basic concepts and network theorems</b> Types of Sources, Loop analysis, Nodal analysis with independent DC and AC Excitations. (Textbook 1: 2.3, 4.1, 4.2, 4.3, 4.4, 10.6) Super position theorem, Thevenin's theorem, Norton's Theorem, Maximum Power transfer Theorem. (Textbook 2: 9.2, 9.4, 9.5, 9.7)	
<b>Teaching-Learning Process</b>	Chalk and Talk, YouTube videos, Demonstrate the concepts using circuits <b>RBT Level:</b> L1, L2, L3

<b>Module-2</b>	
<b>Two port networks:</b> Short- circuit Admittance parameters, Open- circuit Impedance parameters, Transmission parameters, Hybrid parameters (Textbook 3: 11.1, 11.2, 11.3, 11.4, 11.5) <b>Laplace transform and its Applications:</b> Step Ramp, Impulse, Solution of networks using Laplace transform, Initial value and final value theorem (Textbook 3: 7.1, 7.2, 7.4, 7.7, 8.4)	
<b>Teaching-Learning Process</b>	Chalk and Talk <b>RBT Level:</b> L1, L2, L3
<b>Module-3</b>	
<b>Basic Concepts and representation:</b> Types of control systems, effect of feedback systems, differential equation of physical systems (only electrical systems), Introduction to block diagrams, transfer functions, Signal Flow Graphs (Textbook 4: Chapter 1.1, 2.2, 2.4, 2.5, 2.6)	
<b>Teaching-Learning Process</b>	Chalk and Talk, YouTube videos <b>RBT Level:</b> L1, L2, L3



Module-4	
<b>Time Response analysis:</b> Time response of first order systems. Time response of second order systems, time response specifications of second order systems (Textbook 4: Chapter 5.3, 5.4) <b>Stability Analysis:</b> Concepts of stability necessary condition for stability, Routh stability criterion, relative stability Analysis (Textbook 4: Chapter 5.3, 5.4, 6.1, 6.2, 6.4, 6.5)	
<b>Teaching-Learning Process</b>	Chalk and Talk, Any software tool to show time response <b>RBT Level:</b> L1, L2, L3
Module-5	
<b>Root locus:</b> Introduction the root locus concepts, construction of root loci (Textbook 4: 7.1, 7.2, 7.3) <b>Frequency Domain analysis and stability:</b> Correlation between time and frequency response and Bode plots (Textbook 4: 8.1, 8.2, 8.4) <b>State Variable Analysis:</b> Introduction to state variable analysis: Concepts of state, state variable and state models. State model for Linear continuous –Time systems, solution of state equations. (Textbook 4: 12.2, 12.3, 12.6)	
<b>Teaching-Learning Process</b>	Chalk and Talk, Any software tool to plot Root locus, Bode plot <b>RBT Level:</b> L1, L2, L3

**Suggested Learning Resources:****Text Books**

1. Engineering circuit analysis, William H Hayt, Jr, Jack E Kemmerly, Steven M Durbin, Mc Graw Hill Education, Indian Edition 8e.
2. Networks and Systems, D Roy Choudhury, New age international Publishers, second edition.
3. Network Analysis, M E Van Valkenburg, Pearson, 3e.
4. Control Systems Engineering, I J Nagrath, M. Gopal, New age international Publishers, Fifth edition.
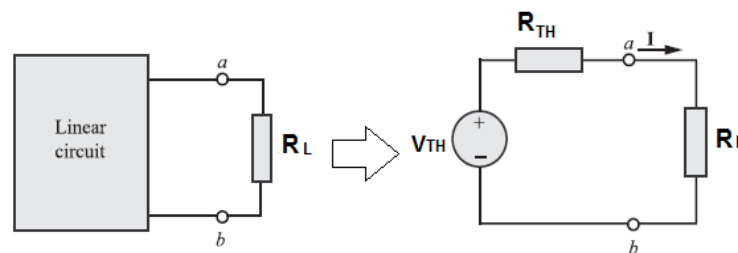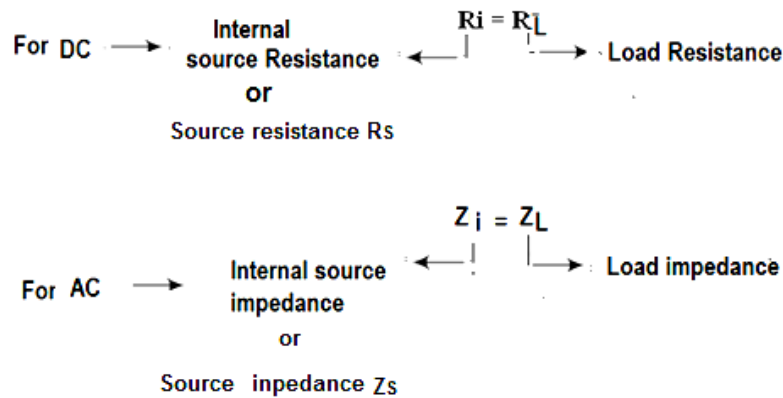
### T2-9.7 MAXIMUM POWER TRANSFER THEOREM

**Maximum power transfer theorem** states that in a linear bidirectional two terminal network Maximum power will be transferred from source to the load when the internal resistance of the source is equal to the load resistance



According to Maximum Power Transfer Theorem, for maximum power transfer from the network to the load resistance,  $R_L$  must be equal to the source resistance i.e. Network's Thevenin equivalent resistance  $R_{TH}$ . I.e.  $R_L = R_{TH}$

The load current  $I$  in the circuit shown above is given by,

$$I = \frac{V_{TH}}{R_{TH} + R_L}$$

The power delivered by the circuit to the load:

$$P = I^2 R = \frac{V_{TH}^2}{(R_{TH} + R_L)^2} R_L$$

$$P = V_{TH}^2 \left\{ \frac{R_L}{(R_{TH} + R_L)^2} \right\}$$

The condition for maximum power transfer can be obtained by differentiating the above expression for power delivered with respect to the load resistance and equating it to zero

$$\frac{dP}{dR_L} = 0$$

$$= \frac{V_{TH}^2}{(R_{TH} + R_L)^4} \left[ (R_{TH} + R_L)^2 (1) - R_L \times 2 (R_{TH} + R_L) (1) \right] = 0$$

$$(R_{TH} + R_L)^2 - R_L \times 2 (R_{TH} + R_L) = 0$$

$$(R_{TH} + R_L) [ (R_{TH} + R_L) - 2R_L ] = 0$$

$$(R_{TH} + R_L) (R_{TH} - R_L) = 0$$

$$(R_{TH} - R_L) = 0$$

$$\therefore \boxed{R_L = R_{TH}}$$

$\frac{dU/V}{dt} = \frac{V \cdot \frac{dU}{dt} - U \cdot \frac{dV}{dt}}{V^2}$

**Source Resistance = Load Resistance**

**This is the condition for max. power transfer**

**The value of Maximum Power Transfer**

$$P = I^2 R = \frac{V_{TH}^2}{(R_{TH} + R_L)^2} R_L$$

**For maximum power transfer  $R_{TH} = R_L$**

$$P_{MAX} = \frac{V_{TH}^2}{(R_L + R_L)^2} \times R_L = \frac{V_{TH}^2}{4R_L}$$

Under the condition of maximum power transfer, the power delivered to the load is given by

$$P_{MAX} = \frac{V_{TH}^2}{4R_L} \text{ Watts}$$

### Efficiency at maximum power transfer

$$P_{OUT} = \text{Output power at max. Power transfer} = P_{MAX} = \frac{V_{TH}^2}{4R_L} \text{ Watts}$$

$$\text{Input power} = P_I = V_{TH} \times \frac{V_{TH}}{R_{TH} + R_L} \text{ Watts}$$


$$\text{For maximum power transfer } R_{TH} = R_L$$

$$\therefore P_{IN} = \text{Power Input} = \frac{V_{TH}^2}{2R_L} \text{ Watts}$$


$$\text{Efficiency} = \eta = \frac{\text{output}}{\text{input}} = \frac{P_{OUT}}{P_{IN}} = \frac{\frac{V_{TH}^2}{4R_L}}{\frac{V_{TH}^2}{2R_L}} = \frac{1}{2} = 50\%$$

Therefore efficiency is 50% at maximum power transfer

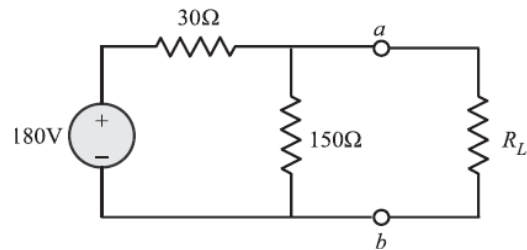1) Find the load  $R_L$  that will result in maximum power delivered to the load for the circuit of Fig. Also determine the maximum power  $P_{max}$ .



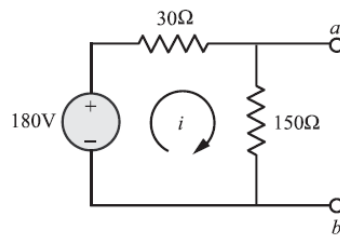
**First step Disconnect the load resistor  $R_L$  and find  $V_{TH}$**




$$i = \frac{180}{150 + 30} = 1\text{ A}$$

$$V_{oc} = V_{TH} = 150 \times i = 150\text{ V}$$

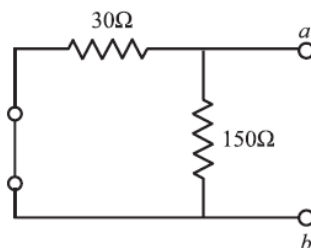**To find  $R_{TH}$  deactivate the independent source**



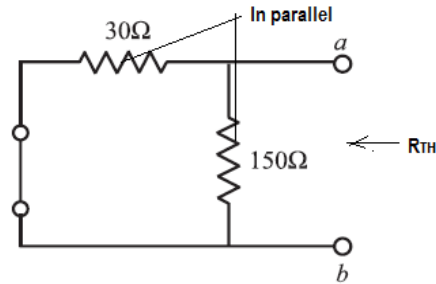


$$R_{TH} = R_{ab} = 30\ \Omega || 150\ \Omega$$

$$= \frac{30 \times 150}{30 + 150} = 25\ \Omega$$

Maximum power transfer is obtained when

$$R_L = R_{TH} = 25\ \Omega.$$

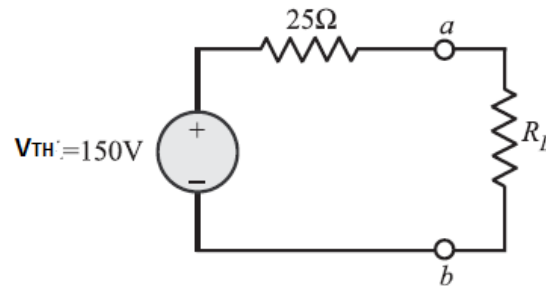


Then the maximum power is


$$P_{max} = \frac{V_{TH}^2}{4R_L} = \frac{(150)^2}{4 \times 25}$$

$$= 2.25\ \text{Watts}$$

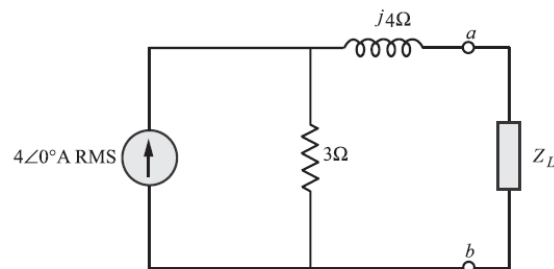
**2) Find the load impedance that transfers the maximum average power to the load and determine the maximum average power transferred to the load ZL shown in Fig.**



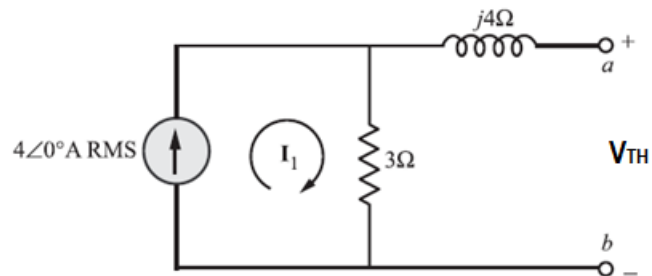**First step disconnect the load resistance**




**Find the  $V_{TH}$**

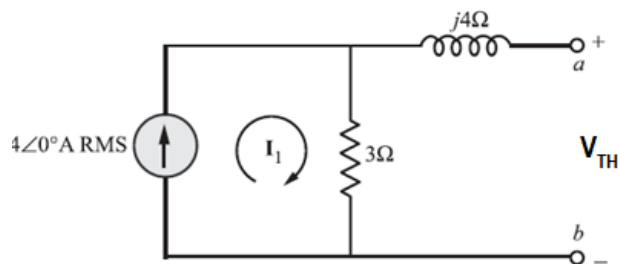

$$V_{TH} = V_{oc} = 4 \angle 0^\circ \times 3$$
$$= 12 \angle 0^\circ \text{ Volts}$$

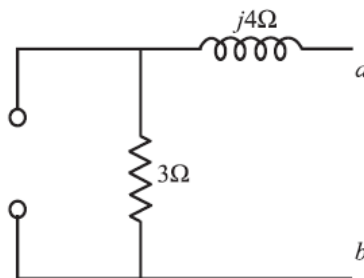**To find  $Z_{TH}$ , deactivate all the**






$$Z_{TH} = 3 + j4 \Omega$$

For maximum power transfer  $Z_{TH} = Z_L$

Therefore  $Z_L = 3 + j4 \Omega$

For maximum average power transfer to the load,  $Z_{TH} = Z_L^* = 3 - j4$ .

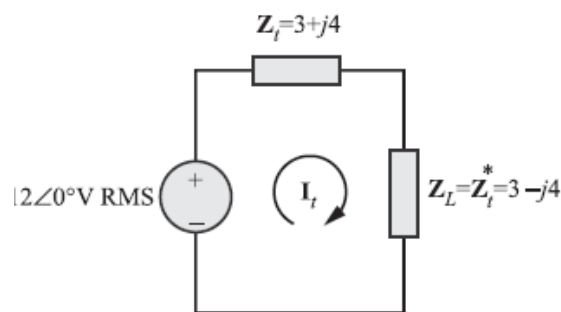For maximum average power transfer, the load impedance  $Z_L$  must be equal to the complex conjugate of the Thevenin impedance  $Z_{TH}$ .




$$\therefore I_{TH} = \frac{12 \angle 0^\circ}{3 + j4 + 3 - j4} = 2 \angle 0^\circ \text{ A}$$


Hence, maximum average power delivered to the load is

$$P = |I_t|^2 R_L = 4(3) = 12 \text{ W}$$

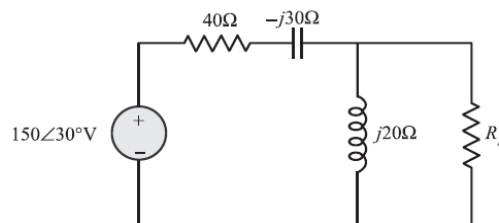3) Refer the circuit given in Fig. Find the value of  $R_L$  that will absorb the maximum average power.



Disconnecting the load resistor  $R_L$


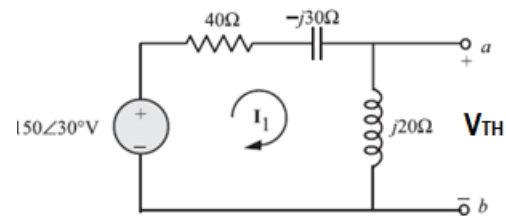


$$V_{TH} = V_{oc} = I_1 (j20)$$

$$= \frac{150 \angle 30^\circ \times j20}{(40 - j30 + j20)}$$

$$= 72.76 \angle 134^\circ \text{ Volts.}$$

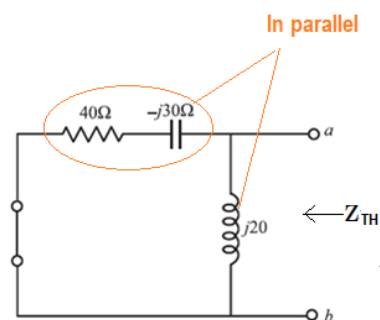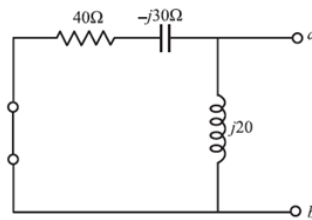**To find  $Z_{TH}$  deactivate the independent source**




$$Z_{TH} = (40 - j30) \parallel j20$$

$$= \frac{j20(40 - j30)}{j20 + 40 - j30} = (9.412 + j22.35) \Omega$$

**The Value of  $R_L$  that will absorb the maximum average power is**

$$R_L = |Z_t| = \sqrt{(9.412)^2 + (22.35)^2}$$

$$= 24.25 \Omega$$

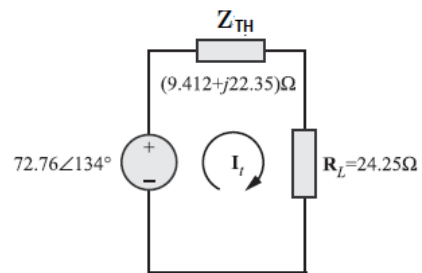

$$I_{TH} = \frac{72.76 \angle 134^\circ}{(9.412 + j22.35 + 24.25)} = 1.8 \angle 100.2^\circ \text{ A}$$

Maximum average power absorbed by RL is

$$P_{\max} = \frac{1}{2} |I_{TH}|^2 R_L$$

$$\begin{aligned} P_{\max} &= \frac{1}{2} (1.8)^2 \times 24.25 \\ &= 39.29 \text{ W} \end{aligned}$$

.....